

NAME:
GT ID #:


SOLUTIONS

Prob 1 (10 points):

The state transition table of a 3-state FSM (2 flip flops) is given below. The state AB = 11 is unused.

Present State = A(t), B(t)		Input = I	Next State = A(t+1), B(t+1)		Output = Z
0	0	0	0	1	0
0	0	1	1	0	1
0	1	0	1	0	0
0	1	1	0	0	1
1	0	0	0	0	1
1	0	1	0	1	0
1	1	0	X (1)	X (0)	X (1)
1	1	1	X (0)	X (1)	X (0)

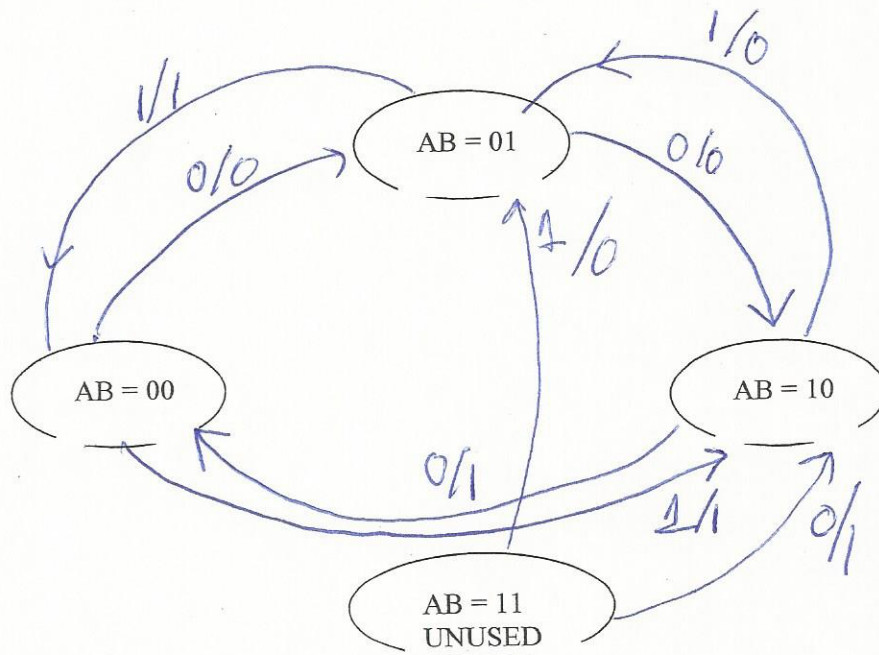(a) Draw its state transition diagram below.



(b) You are to design a finite state machine that realizes the above state transition diagram/state transition with D flip flops. Below, fill in the K-maps for $D(A)$, $D(B)$ and Z (see figure on next page) and write the minimal Boolean expressions for the same. Make sure that the machine is not caught in a self-loop if it starts up in the state $AB=11$.

		BI			
		00	01	11	10
A	0	0	1	0	1
	1	0	0	X	X

$$D(A) = \overline{A} \overline{B} I + B \overline{I}$$


		BI			
		00	01	11	10
A	0	1	0	0	0
	1	0	1	X	X

$$D(B) = \overline{A} \overline{B} \overline{I} + A I$$

		BI			
		00	01	11	10
A	0	0	1	1	0
	1	1	0	X	X

$$Z = \overline{A} I + A \overline{I}$$

(c) Draw a circuit diagram for the finite state machine showing all logic, FSM input and output and the two D flip flops corresponding to A and B.

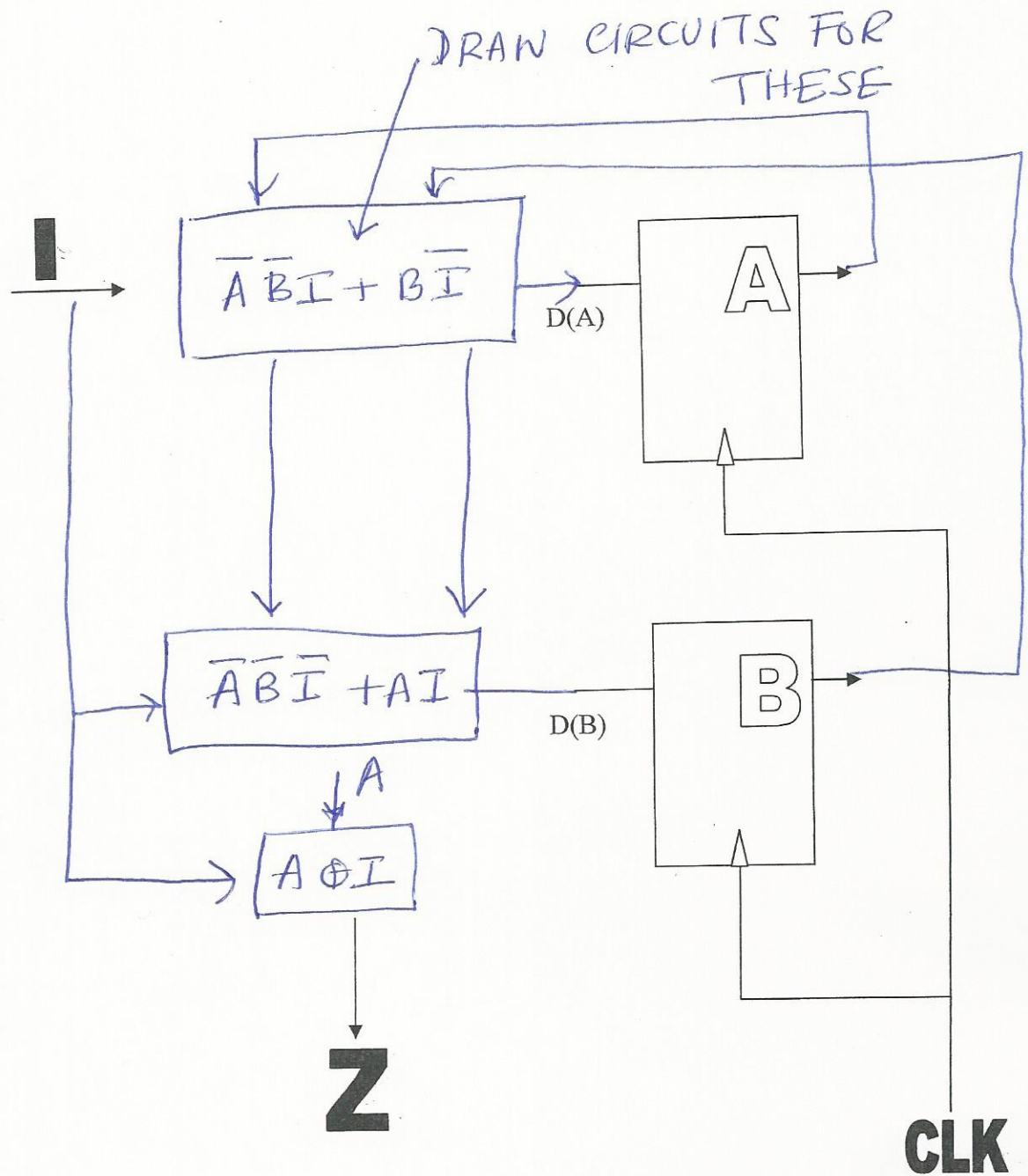

Prob 2. (10 points)

A FSM has two flip flops with outputs A and B and inputs D(A) and D(B) respectively (as in the previous problem, part (c)). The FSM has an input I and one output Z (as in the previous problem). The equations for the FSM are given below. The flip flops are **positive edge** triggered.


$$D(A) = (A + B) \oplus I \quad (\oplus = \text{XOR, XOR} = \text{exclusive OR})$$

$$D(B) = \bar{A} \oplus B \quad (\text{note again, } D(B) = ((A \text{ bar}) \text{ XOR } B) !)$$

$$Z = B + I$$

Initially, at $t=0$, $A(0) = B(0) = 0$.

 Draw the waveforms for the outputs of the flip flops corresponding to A and B and the output Z below, given the waveform for the input I.



Prob 3 (10 points)

Consider the following truth table of 4 input variables.

W	X	Y	Z	F = f(W,X,Y,Z)
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

$$WY = 00$$

XZ	F
00	0
01	1
10	1
11	0

$$F = X \oplus Z$$

$$WY = 10$$

XZ	F
00	1
01	1
10	1
11	0

$$F = \overline{X \cdot Z}$$

$$WY = 01$$

XZ	F
00	1
01	0
10	0
11	0

$$F = \overline{(X+Z)}$$

$$WY = 11$$

XZ	F
00	0
01	1
10	0
11	0

$$F = \overline{X}Z$$

You are to realize this truth table using a 4-to-1 mux with control signals connected to W and Y (see Figure) and additional logic whose inputs are driven by the signals X and Z. Please draw your circuit (additional logic) below and show all steps.

